
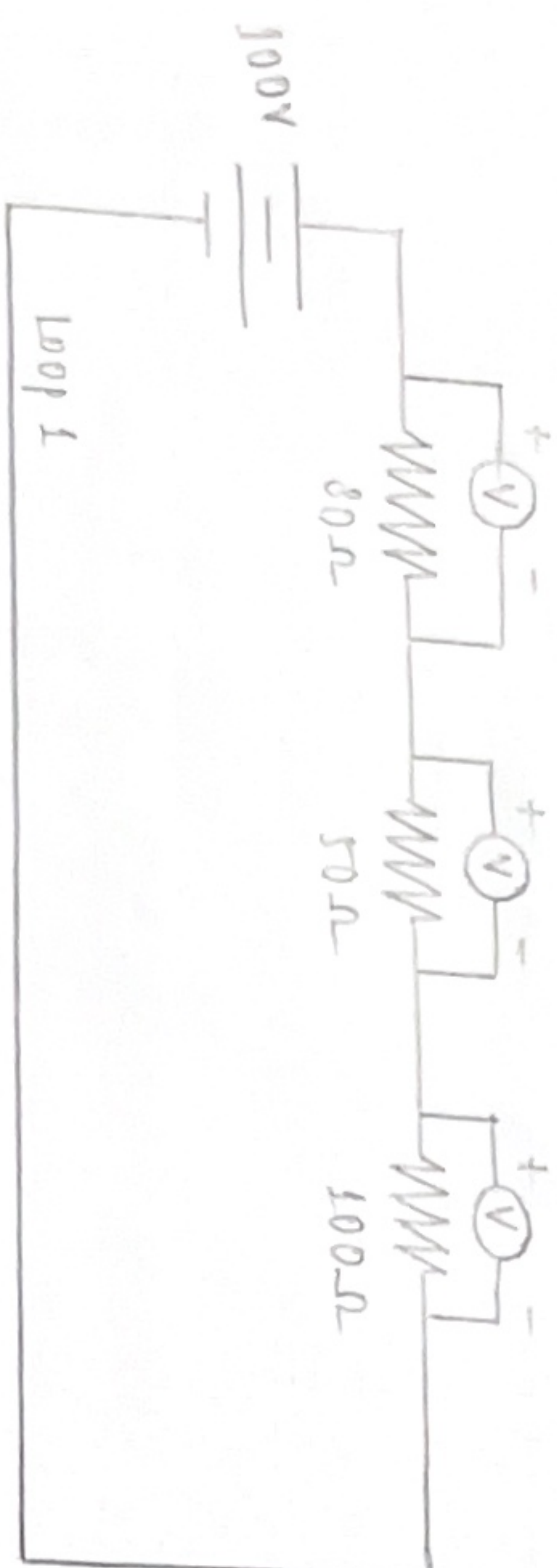


CIRCUIT:

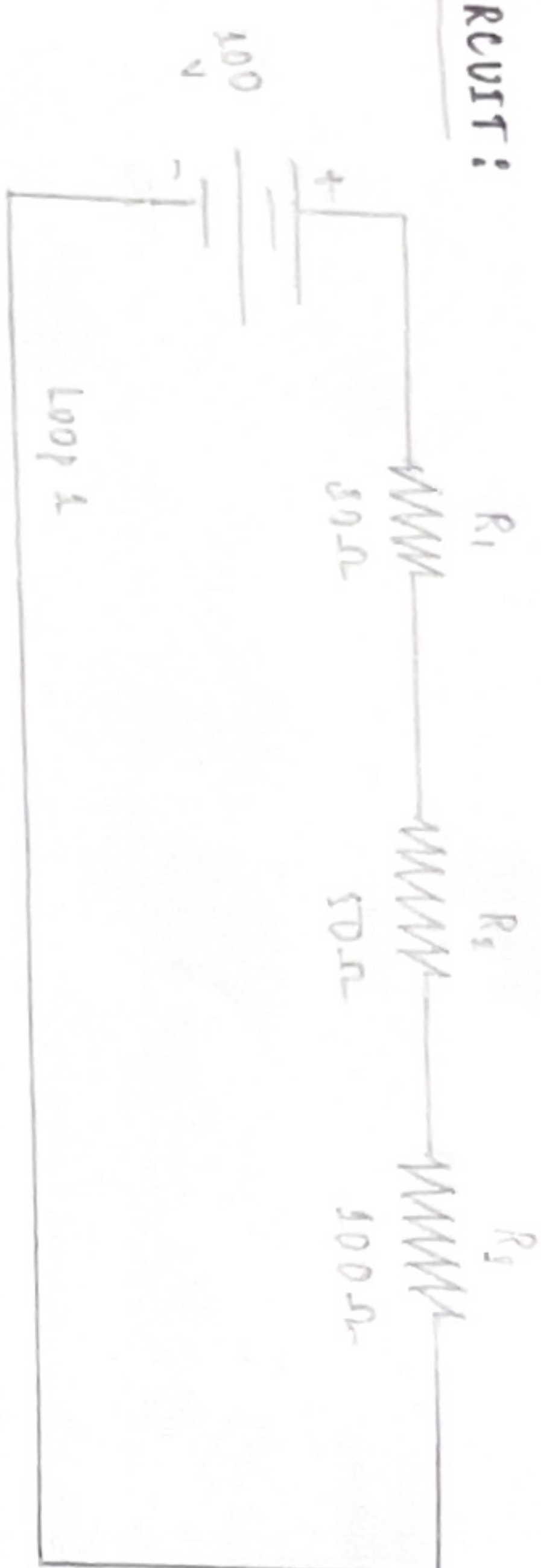

TABULATION:

KVL	Source (V)	$V_{30\Omega}$ (V)	$V_{50\Omega}$ (V)	$V_{100\Omega}$ (V)	$V_{30\Omega} + V_{50\Omega} + V_{100\Omega}$ (V)
Theoretical	100	16.68V	27.8V	55.6V	100.05
Practical	100	16.7V	27.8V	55.6V	100.1

Expt. No. 01

Page No. 02

VERIFICATION OF KIRCHOFF'S VOLTAGE LAW AND KIRCHOFF'S

CURRENT LAW

AIM:

To verify Kirchhoff's voltage law for loop 1 and Kirchhoff's current law in node A for the following circuit.

APPARATUS REQUIRED:

laptop and proteus software.

THEORY:

According to Kirchhoff's voltage law sum of potential raised are equal to sum of potential drop in a loop.

In loop 1 by KVL:

$$V = V_1 + V_2 + V_3 \rightarrow \text{①}$$

$$100 = IR_1 + IR_2 + IR_3$$

$$R_{eq} = R_1 + R_2 + R_3$$

$$R_{eq} = 30 + 50 + 100$$

$$R_{eq} = 180\Omega$$

$$I = \frac{V}{R_{eq}} = \frac{100}{180} = 0.556A$$

$$V_1 = V_{30\Omega} = IR_1 = 0.556 \times 30 = 16.68V$$


$$V_2 = V_{50\Omega} = IR_2 = 0.556 \times 50 = 27.8V$$

$$V_3 = V_{100\Omega} = IR_3 = 0.556 \times 100 = 55.6V$$

Substitute V_1 , V_2 and V_3 values in ①

$$100 = 16.68 + 27.8 + 55.6$$

CIRCUIT:

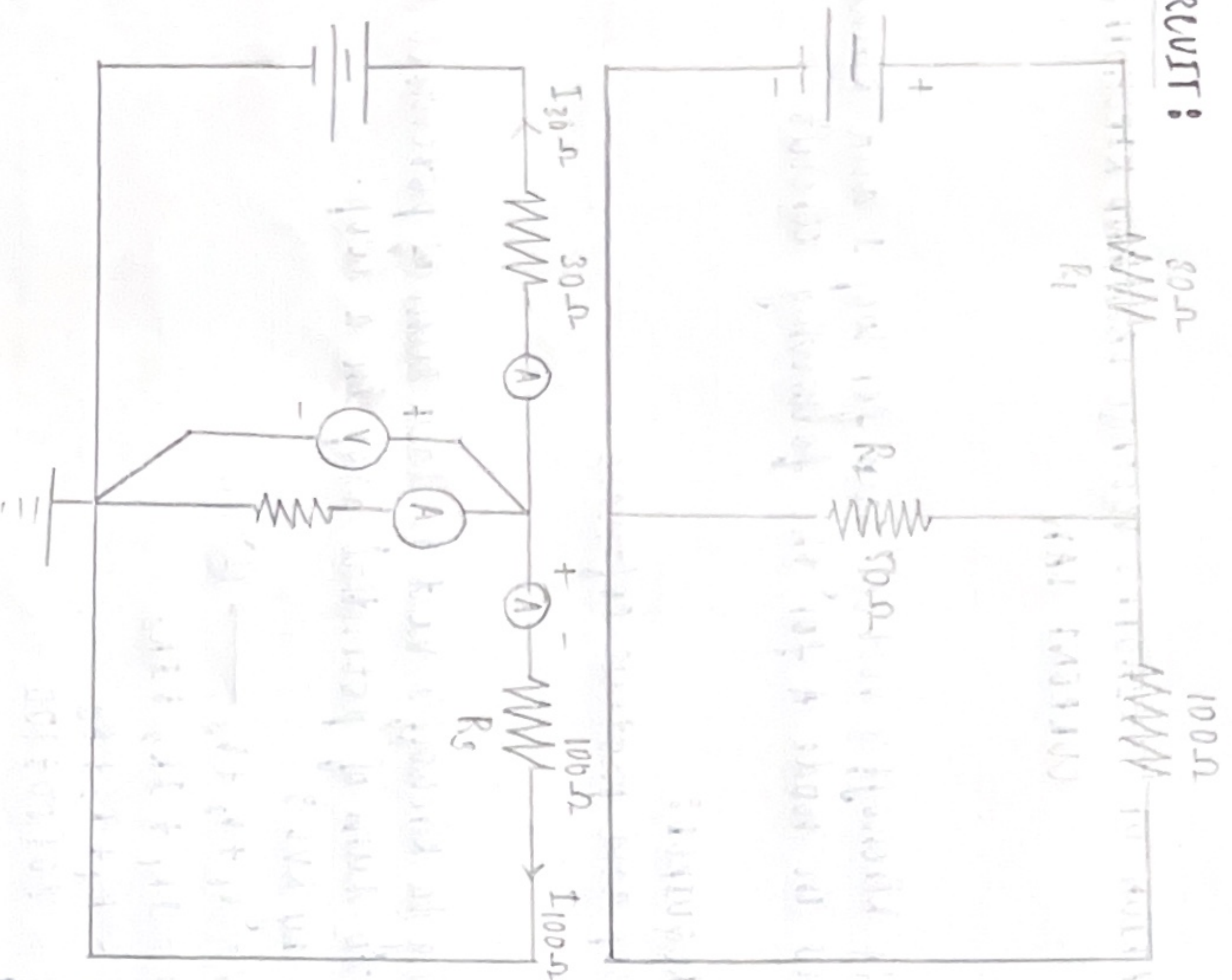

TABULATION:

KCL	$I_{30\Omega}$	$I_{50\Omega}$	$I_{100\Omega}$	V_A
Theoretical	-1.48 A	1.85 A	0.56 A	52.63 V
Practical	1.58 A	1.05 A	0.53 A	52.6 V

Expt. No.

01

Page No.

04

$$100V = 100V$$

Hence Proved.

Kirchoff's current law:

In a junction, Incoming current is equal to outgoing current.

At node A

$$I_{30\Omega} + I_{50\Omega} + I_{100\Omega} = 0$$

$$\frac{V-100}{30} + \frac{V}{50} + \frac{V}{100} = 0$$

$$V \left[\frac{1}{30} + \frac{1}{50} + \frac{1}{100} \right] - \frac{100}{30} = 0$$

$$V [0.0633] - 3.333 = 0$$

$$V = 3.333$$



$$0.0633$$

$$V = 52.63V$$

$$I_{30\Omega} = \frac{V-100}{30} = \frac{52.63-100}{30} = -1.58A$$

$$I_{50\Omega} = \frac{V}{50} = \frac{52.63}{50} = 1.05A$$
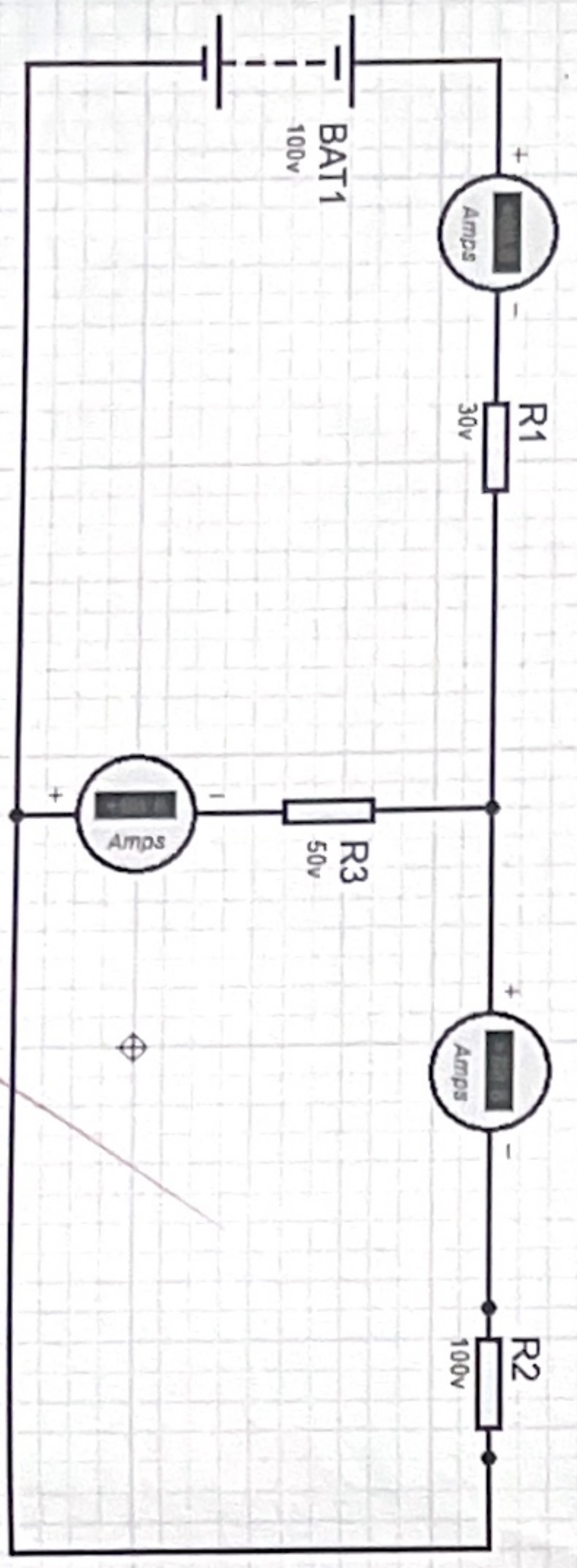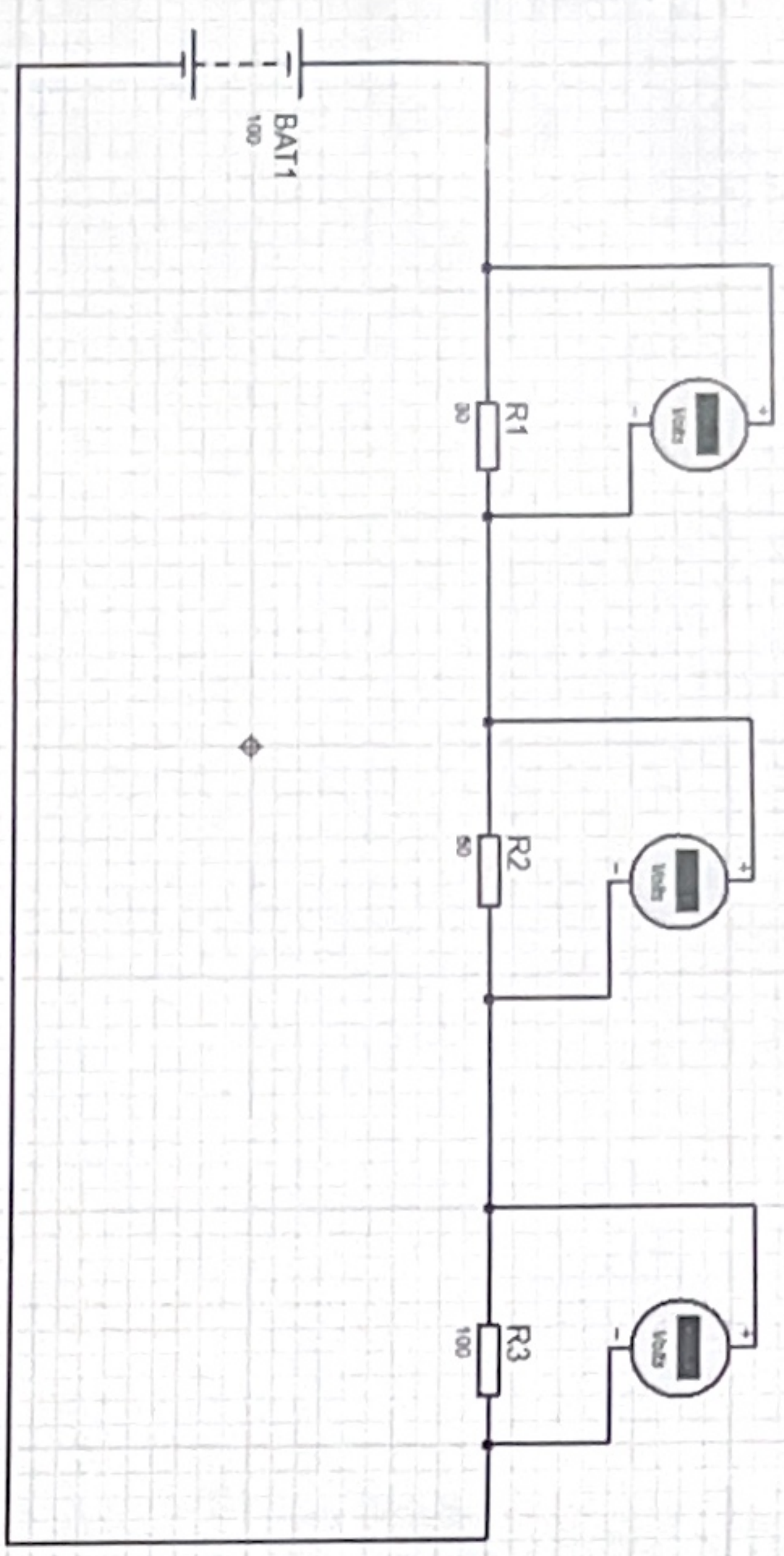
$$I_{100\Omega} = \frac{V}{100} = \frac{52.63}{100} = 0.53A$$



Expt. No.

01

Page No.

06

At node A

$$I_{30\Omega} + I_{50\Omega} + I_{100\Omega} = 0$$

$$-1.58 + 1.05 + 0.58 = 0$$

Hence Proved.

RESULT:

Thus, the Kirchhoff's voltage law and Kirchhoff's current law has been verified successfully.

99 ✓
20/02/22

